

RRAM-Based Analog Circuit for Matrix Inversion: Simulation and Analysis

Marco Mura

Outline

- RRAM-based Matrix Inversion Circuit
- Simulation and Results
- Final Remarks

RRAM-Based Matrix Inversion Circuit

The Linear Inverse Problem

$$Ax = y$$

$$\rightarrow x = A^{-1}y$$

$$A \text{ } nxn , \det(A) \neq 0$$


Matrix Inversion in Digital Computer

Latency



High Energy Dissipation

 RRAM-Based Analog Circuit for Matrix Inversion



$A \rightarrow G$

Kirchhoff's current law

Source: "Invited Tutorial: Analog Matrix Computing With Cross point Resistive Memory Arrays", Sun and Ielmini, 2022.

Analog vs Digital

High speed
Low power



BUT




Non-idealities:
Accuracy degradation



Simulation and Results




Workflow

   


Evaluation of Encoding Strategies under Variability and RTN Effects

 Evaluation of Encoding Strategies under Variability and RTN Effects: I_{comp} , V_{reset}




Evaluation of Encoding Strategies under Variability and RTN Effects: **Icomp**, **Vreset**

Compliance current

 


V RESET

 


Evaluation of Encoding Strategies under Variability and RTN Effects: **Icomp**, **Vreset**

Compliance Current Encoding

 


V Reset Encoding

 


Evaluation of Encoding Strategies under Variability and RTN Effects: I_{comp} , V_{reset}

Compliance current

 


NRMSE = 0,0822

V_{RESET}

 


NRMSE = 0,7358

 Evaluation of Encoding Strategies under Variability and RTN Effects: Multiple Devices




Evaluation of Encoding Strategies under Variability and RTN Effects: Multiple Devices

Compliance current

 


Compliance current,
2 devices per weight

 


Evaluation of Encoding Strategies under Variability and RTN Effects: Multiple Devices


Compliance current

 

Compliance current,
2 devices per weight

 


Effects of Line Parasitic Resistances

 


Effects of Line Parasitic Resistances


5x5 crossbar

 

10x10crossbar

 


 Handling Matrices with Positive and Negative Entries




Handling Matrices with Positive and Negative Entries

Current compliance

 

Power Consumption Estimation

 

$$V_{read} \leq 0.01V$$

5x5 basic circuit \sim tens μW

More complex circuit \sim hundreds μW

Source: "Invited Tutorial: Analog Matrix Computing With Cross point Resistive Memory Arrays", Sun and Ielmini, 2022.

Final Remarks

Final Remarks

Promising alternative



Non-idealities



Bibliography

- [1] Zhong Sun and Daniele Ielmini. "Invited Tutorial: Analog Matrix Computing With Cross point Resistive Memory Arrays". In: IEEE Transactions on Circuits and Systems II: Ex-press Briefs 69.7 (2022).